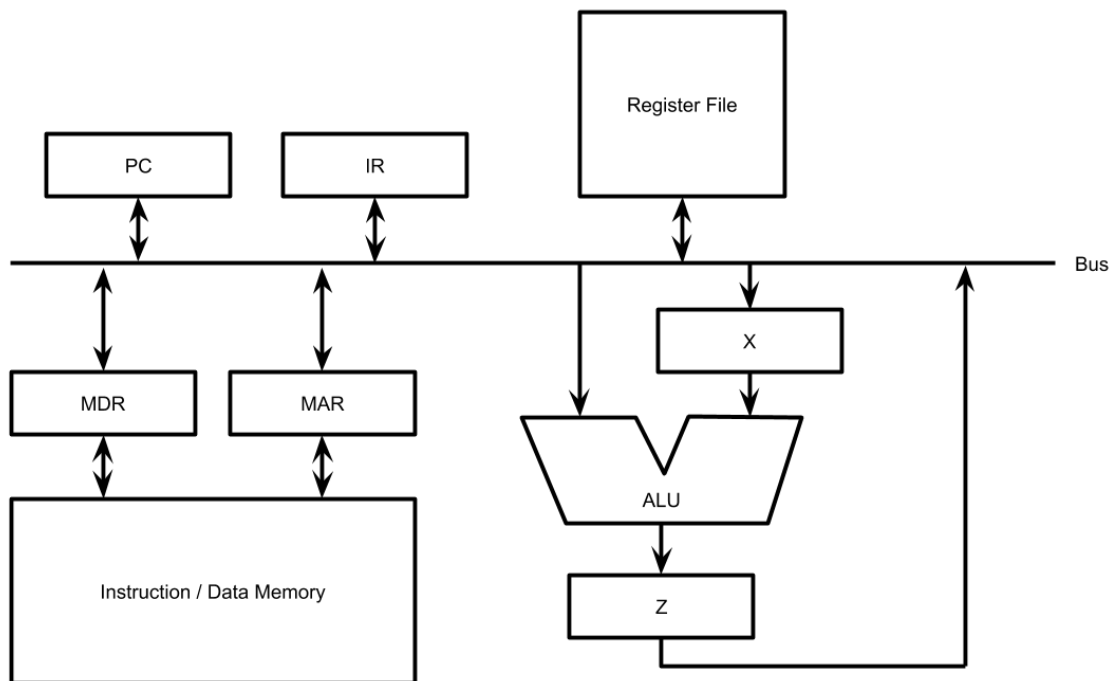


1. Building a computer from parts
 - a. You know enough at this point to build your own computer
 - i. Add two numbers
 1. Use an adder to do so
 - ii. Implement other operations like subtract, AND, OR, XOR, so on
 1. Use those components, combine all the above into one unit (an ALU)
 2. Need to pick between them, so MUX / switch to tell us what to do
 - iii. Calculate a running sum of numbers
 1. Need storage and state logic
 2. Otherwise, use ALU to calculate values
 - iv. Add based on values stored somewhere
 1. Need storage, registers (from sequential design) to hold stored values, and state logic
 2. Otherwise, use ALU to calculate values
2. Von Neumann architecture
 - a. Almost all current machine designs based on concepts developed by John von Neumann
 - i. Will follow the same when building our own CPU in Lab 3
 - b. Architecture based on following three key concepts
 - i. Data and instructions stored in single read/write memory
 - ii. Contents of said memory addressable by location
 1. Doesn't matter what type of data is there
 - iii. Execution of a program occurs sequentially
 1. To change this, order must be explicitly modified
3. Tasks of a computer (from before)
 - a. Move data – in and out of the machine, using input registers
 - b. Process data – ALU does this
 - c. Store data – bunch of different places
 - i. Registers in the CPU
 - ii. RAM
 - iii. Other ones we'll talk about later
 1. CPU cache, which is a subset of RAM
 2. Backing storage, like hard drives (HDDs)
 - d. Control – switches and MUXes
4. Putting together a basic CPU
 - a. Need to add registers to hook up to our ALU
 - i. ALU must store values somewhere
 - ii. Could have direct paths from ALU to registers to store values
 1. This is expensive, though
 - iii. Alternative: a *bus*
 1. Collection of low-resistance wires used to transfer information from one place to another (or multiple places)
 2. Analogy: streets
 - a. Each house can have a separate path to Trader Joe's
 - b. More efficient to share the path, which are streets
 3. Bus often has lines for data, lines for addresses, and lines for control
 - a. Inside a CPU, bus only contains data lines
 - b. Control, address lines routed separately

5. Single bus and executing instructions
 - a. Simplistic single bus CPU below



- b. Sequence of actions
 - i. Fetch – need to get instruction at memory location specified by PC into IR
 - 1. PC places its value on bus, MAR takes in value
 - 2. Memory returns desired value at location MAR to MDR
 - 3. MDR places its value on bus, IR takes value in
 - ii. Decode – CPU determines what actions to take
 - 1. Values stored in IR tell CPU exactly what to do
 - 2. “Decode” the IR to determine what steps to take next
 - iii. Execute – run the instruction and generate a value or other action

1. Example – let's add two memory locations and place result in register file
 - a. Address of first operand placed on bus from IR
 - b. MAR takes in value, memory returns desired value to MDR
 - c. MDR places its value on bus, X takes in value for temporary storage
 - d. Address of second operand placed on bus from IR
 - e. MAR takes in value, memory returns desired value to MDR
 - f. MDR places its value on bus
 - g. ALU takes in current value on bus and X, places its output in Z
 - h. Z places its value on bus, register file takes in value
 - i. IR places register address on bus, register file takes in address